

Functional Programming - Lab Class Exercises 5

Frank C Langbein
frank@langbein.org

Version 1.4.0

1. Car Velocity and Acceleration

Assume you have an analog voltage signal x that represents the position of a car. Construct an analog circuit to compute the car's velocity and acceleration. This can be presented as op-amp circuit or analog compute components.

2. Second Order Differential Equation Solver

Consider the second-order linear differential equation $y''(t) = -y'(t) + y(t)$ where y is a scalar function over the real numbers, $y: \mathbb{R} \rightarrow \mathbb{R}$. Design an analog circuit to simulate this equation, assuming $y'(0)$ and $y(0)$ are known. This can be presented as op-amp circuit or analog compute components.